

## Snakegame

with 30 LEDs Charlyplexing methode

# TechDen

### Interne snakegame workshops

Ma 5 juli; Uitleg HW & solderen -> Roland


Ma 19 juli; Uitleg SW principe & Arduino IDE -> Jacko

Ma 2 aug; Zelf applicatie maken & Nadenken hoe externe workshops


## Snakegame HW

- Items:
- Bare Arduino
- 2. Leds control; Charlyplexing
- 3. Buttons & Piezo speaker
- 4. Programming interfaces
  - ICSP; in-circuit serial programming Used for programming bootloader
  - Serial; Needs a FTDI USB->TTL board Used for uploading sketches
- 5. Power Supply
- 6. PCB


#### Bare Arduino

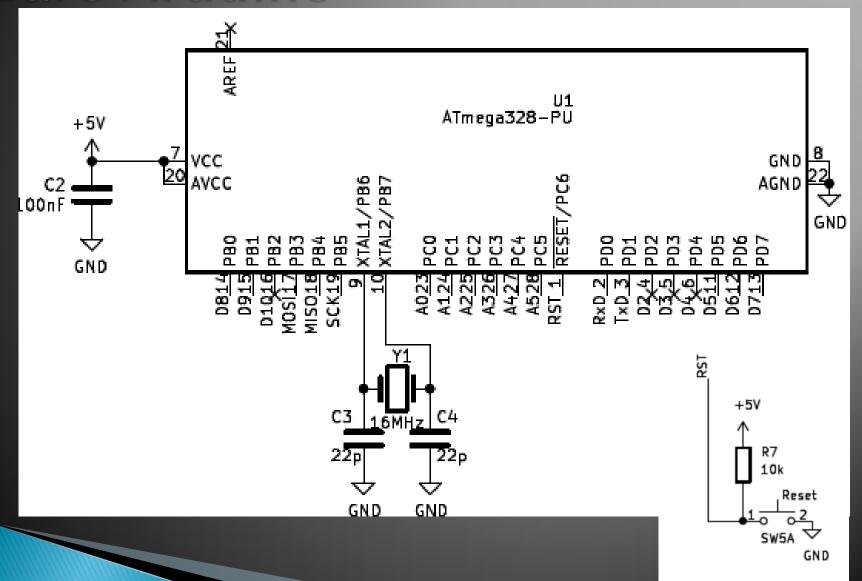

## Multiplexed LED matrix

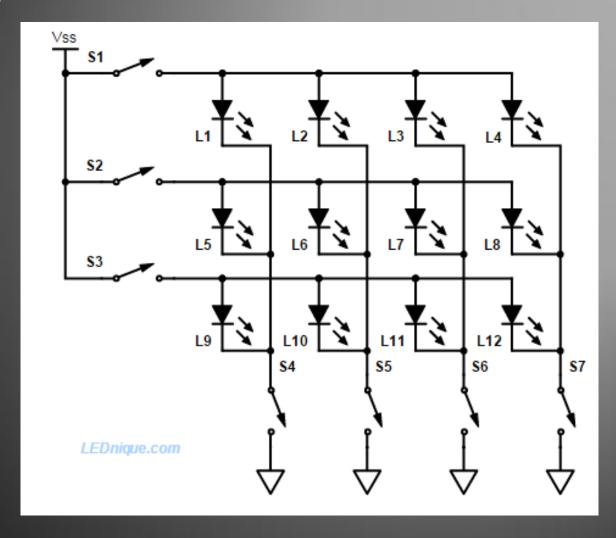


#### Charlyplexed LED matrix

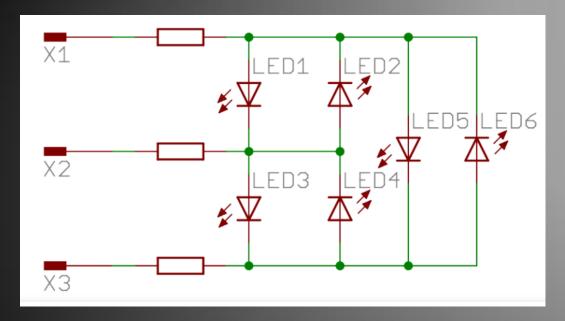


See; Charlyplexing LED matrix

#Leds = N\*(N-1)


#### Charlyplexed LED matrix

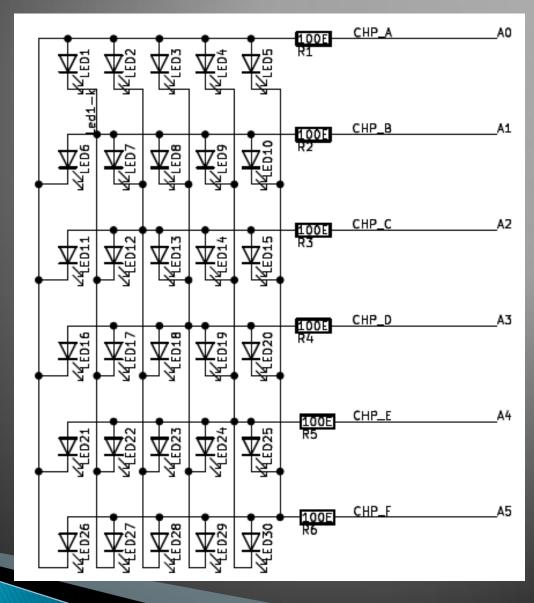


#### Buttons & Piezo speaker

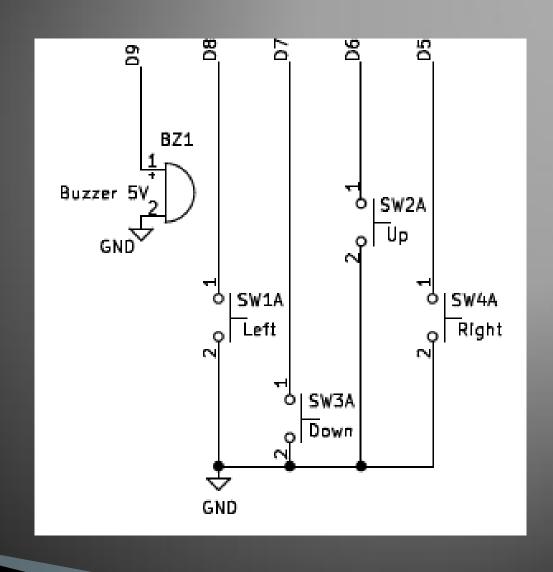


## Programming Interfaces

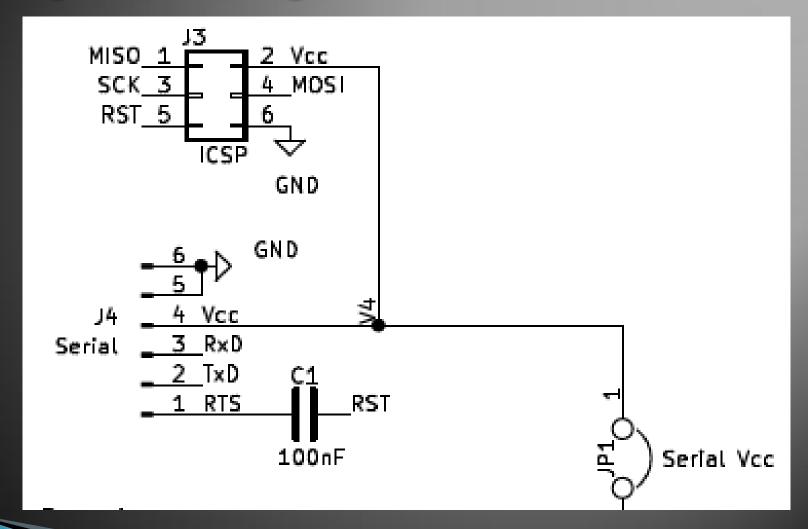


#### External FTDI Board

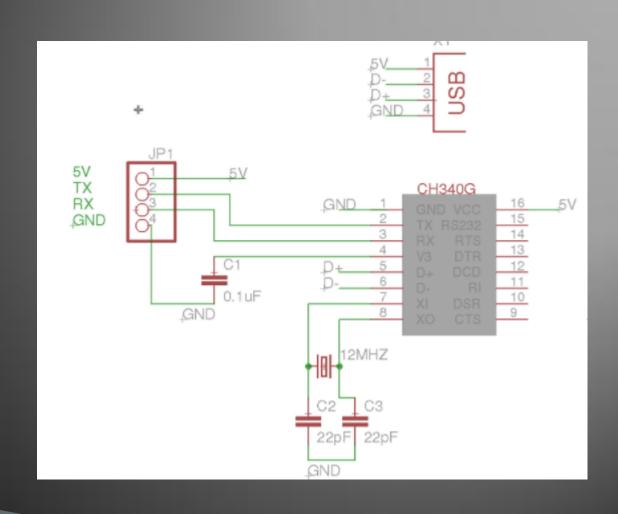


## Power supply

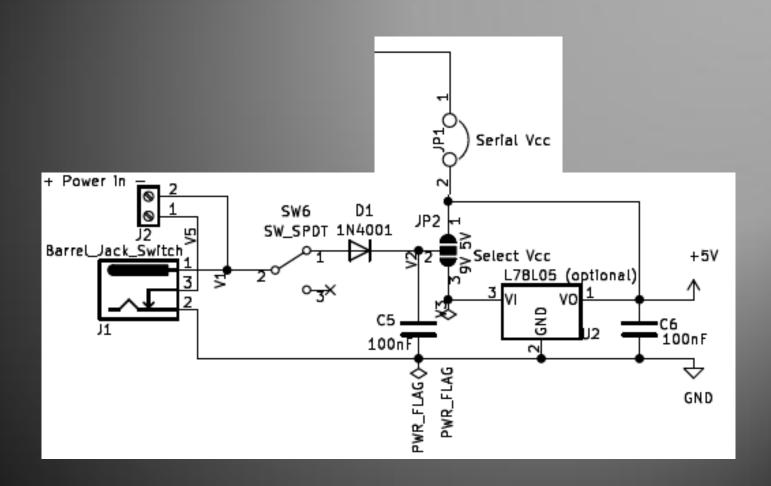

#### PCB

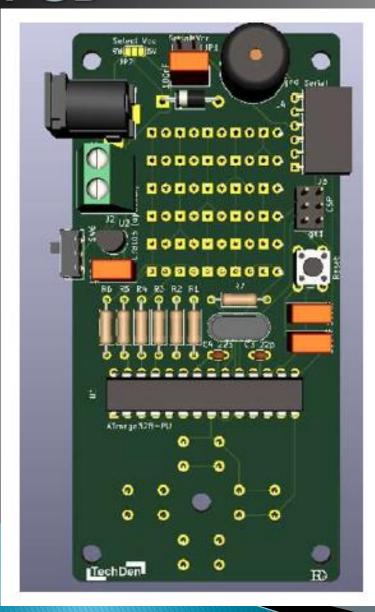

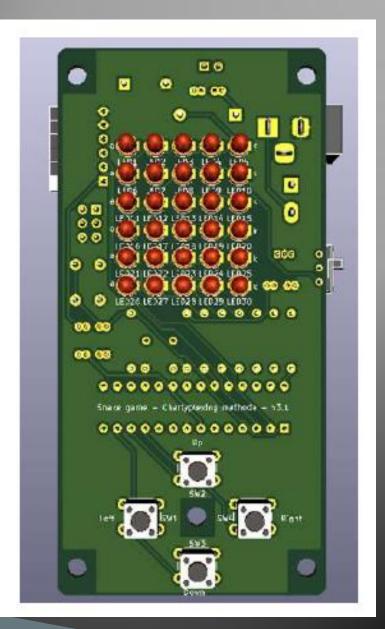

#### Case voorbeeld







Demo

#### Check

- LEDs & 4 Buttons op achterzijde van PCB!!
- Polariteit leds & diode
- Positie ATMEGA328
- Jumpers Power supply
- Positie FTDI boardje

ATMEGA328 is reeds voorzien van bootloader & DEMO sketch